

# Sequential Logic


## Flip-flops and Counter Implementation

# Overview

## Part 2





- Master-Slave D Flip Flop
  - Circuit
  - Propagation Delay
  - Timing Diagram
  - Setup/Hold Time
  - Enable input
  - Reset input
- Counter
  - Truth Table
  - Inverting bits using enable

# Positive-Edge Master-Slave D Flip-Flop

 

# Propagation Delay



- Wire Delay
- Charge/Discharge Delay

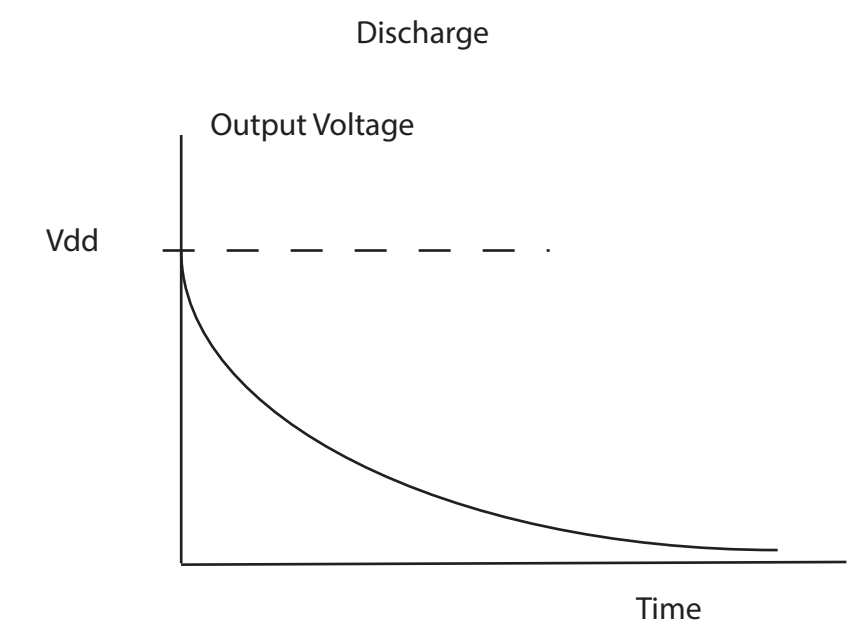   

# Positive-Edge Master-Slave D Flip-Flop
  
## Timing Diagram with Propagation Delay



- Q updates take place only on rising-edge of C (clock) signal



# Positive-Edge Master-Slave D Flip-Flop
  
## Setup Time



- D input need to be stable before C rising edge
- Race condition between D and C
- Avoid uncertainty of output



# Positive-Edge Master-Slave D Flip-Flop

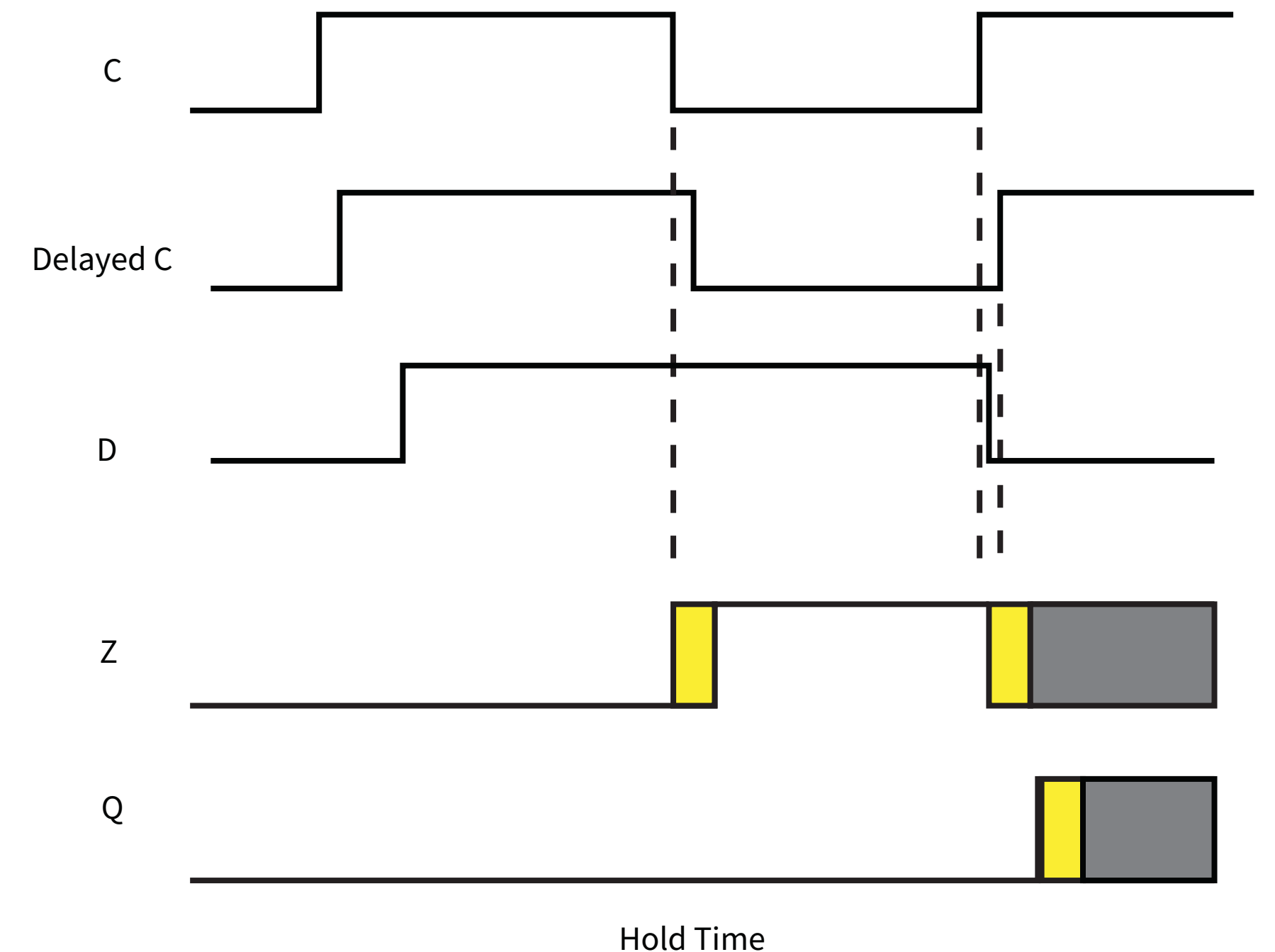 
## Hold Time

- D input need to be stable after C rising edge
- Race condition between D and C
- Avoid uncertainty of output



# Positive-Edge Master-Slave D Flip-Flop


## Standard (Simplified) Representation

 



 
# Flip-flop with enable input

- Enable signal == 0:
  - D input is disabled
  - Flip-flop preserves value
- Enable signal == 1:
  - Allow D input to change Q




# Flip-flop with enable input

## Standard (Simplified) Representation

 

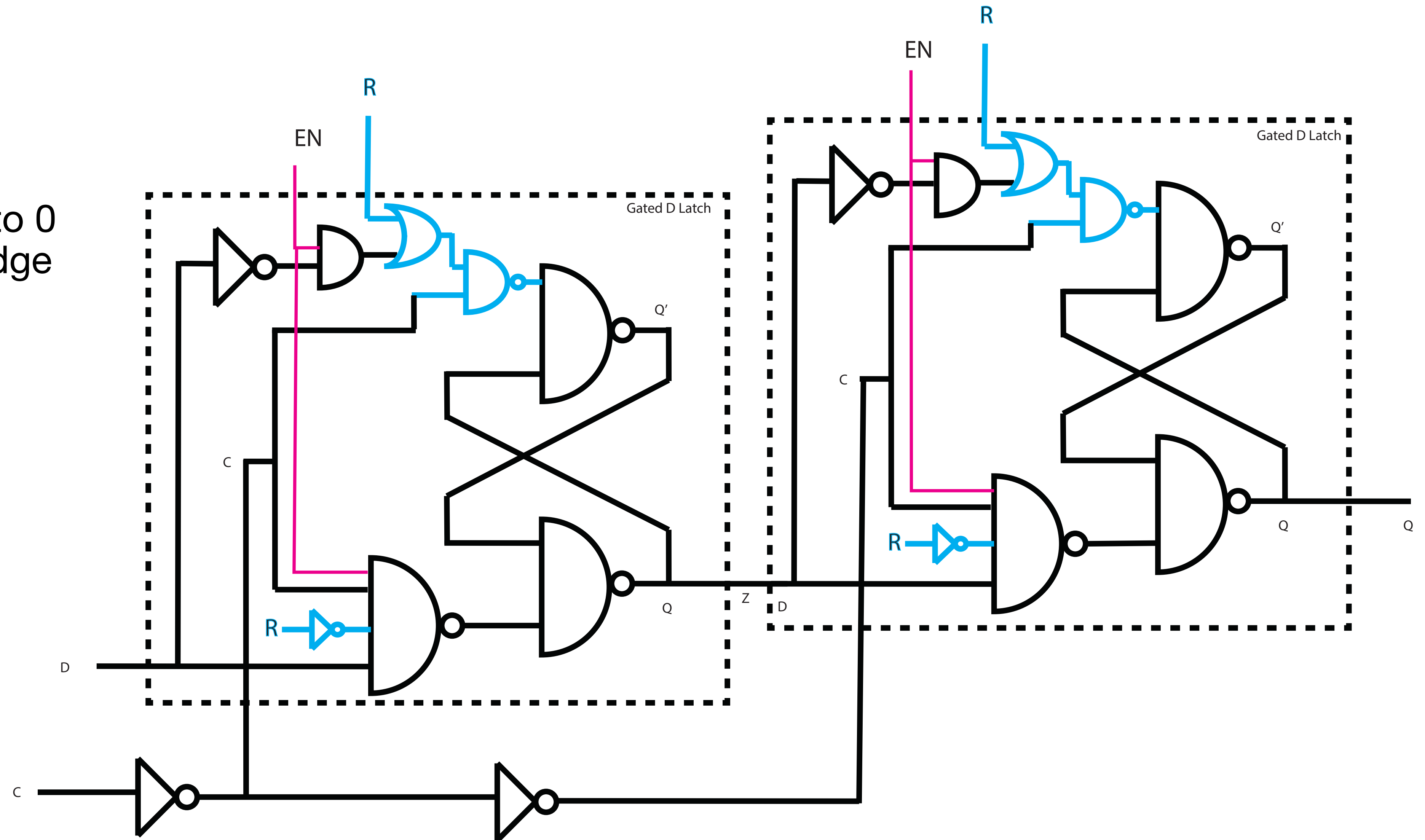
# Flip-flop with reset input

- $R=0$ : No impact
- $R=1$ : clear output to 0 at clock (C) rising edge



# Flip-flop with reset input

## Timing Diagram

 




# Counter

- Use flip-flops to increment value every clock cycle
  - Add 1 to current value of counter
  - Store updated value back in counter

- 3-bit counter values (range 0-7):

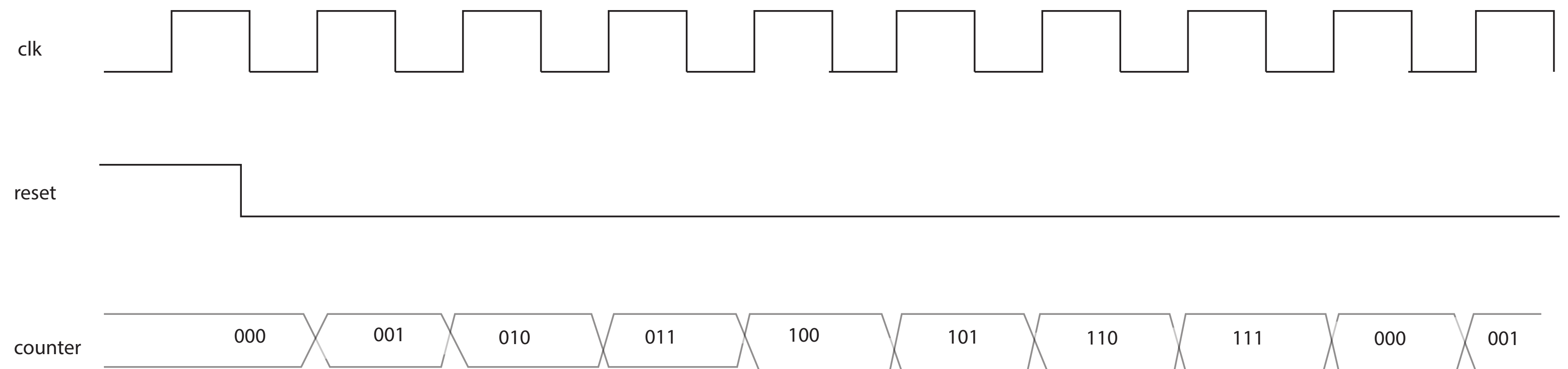- 000
- 001
- 010
- 011
- 100
- 101
- 110
- 111
- 000 (Repeat from 0)
- ...



# Counter

## Truth Table

- Inputs:
  - Counter Old
    - 3-bits
- Outputs:
  - Counter New
    - 3-bits

| Qold Bit 2<br>(Q2) | Qold Bit 1<br>(Q1) | Qold Bit 0<br>(Q0) | Qnew Bit 2 | Qnew Bit 1 | Qnew Bit 0 |
|--------------------|--------------------|--------------------|------------|------------|------------|
| 0                  | 0                  | 0                  | 0          | 0          | 1          |
| 0                  | 0                  | 1                  | 0          | 1          | 0          |
| 0                  | 1                  | 0                  | 0          | 1          | 1          |
| 0                  | 1                  | 1                  | 1          | 0          | 0          |
| 1                  | 0                  | 0                  | 1          | 0          | 1          |
| 1                  | 0                  | 1                  | 1          | 1          | 0          |
| 1                  | 1                  | 0                  | 1          | 1          | 1          |
| 1                  | 1                  | 1                  | 0          | 0          | 0          |

# Counter

## Equations

- $Q_{\text{new Bit 0}} = Q_0'$
- $Q_{\text{new Bit 1}} = Q_1Q_0' + Q_1'Q_0$
- $Q_{\text{new Bit 2}} = Q_2'Q_1Q_0 + Q_2Q_1' + Q_2Q_0'$



# Counter

## Alternate implementation using enable input of flip-flop

- Tie inverted value of flip-flop (Q) to the input (D) of the flip-flop
  - D input of counter bit 2 = inverted value of Q output of counter bit 2
  - D input of counter bit 1 = inverted value of Q output of counter bit 1
  - D input of counter bit 0 = inverted value of Q output of counter bit 0
- Create truth table to see when inversion is needed
  - Enable input of flip-flop controls when the flip-flop is updated

# Counter with enable input register

## Truth Table

| Qold Bit 2<br>(Q2) | Qnew Bit 2 | Invert<br>Bit 2 |
|--------------------|------------|-----------------|
| 0                  | 0          | 0               |
| 0                  | 0          | 0               |
| 0                  | 0          | 0               |
| 0                  | 1          | 1               |
| 1                  | 1          | 0               |
| 1                  | 1          | 0               |
| 1                  | 1          | 0               |
| 1                  | 0          | 1               |

| Qold Bit 1<br>(Q1) | Qnew Bit 1 | Invert<br>Bit 1 |
|--------------------|------------|-----------------|
| 0                  | 0          | 0               |
| 0                  | 1          | 1               |
| 1                  | 1          | 0               |
| 1                  | 0          | 1               |
| 0                  | 0          | 0               |
| 0                  | 1          | 1               |
| 1                  | 1          | 0               |
| 1                  | 0          | 1               |

| Qold Bit 0<br>(Q0) | Qnew Bit 0 | Invert<br>Bit 0 |
|--------------------|------------|-----------------|
| 0                  | 1          | 1               |
| 1                  | 0          | 1               |
| 0                  | 1          | 1               |
| 1                  | 0          | 1               |
| 0                  | 1          | 1               |
| 1                  | 0          | 1               |
| 0                  | 1          | 1               |
| 1                  | 0          | 1               |

# Counter with enable input register

## Equation

- Enable input for counter bit 0: 1
  - Bit 0 changes every clock cycle
- Enable input for counter bit 1:  $Q_0$ 
  - Bit 1 changes every other clock cycle
    - $Q_0 == 1$  (no update when  $Q_0$  is 0)
- Enable input for counter bit 2:  $Q_1Q_0$ 
  - Bit 2 changes every 4th clock cycle
    - $Q_1Q_0 == 11$  (no update when  $Q_1Q_0$  is 00, 01, 10)

# Counter with enable input register

