

# Sequential Logic

## State Machines

# Overview

## Part 3

- Glitch with single output bit and multiple input bits
- Finite State Machine
- Alarm example
  - Glitch
    - Flip-flop for outputs
    - Gray code
  - Mealy vs. Moore

# Glitch

- $Z = A'B' + AC$
- ABC changes from 001 to 101
  - A changes from 0 to 1
- Z should remain at 1
- Glitch: unexpected change in output for a short period of time
  - Z could go to 0 if  $A'B'$  changes from 1 to 0 before AC changes from 0 to 1
- Add  $B'C$  term to avoid glitch
  - $Z = A'B' + AC + B'C$
- Alternative solution:
  - Add a flip-flop for Z to ensure glitch doesn't show up at flip-flop output

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Finite State Machine

## Design Steps

- Obtain requirements of system
- Create state transition diagram
- Identify number of bits needed to store state information
- Assign binary values for each state
- Create truth table
- Use K-Maps to write equation
- Draw block diagram
  - Flip-flops (registers) for each bit of state
  - Combinational logic to update the D input of each bit of state
  - Combinational logic to generate the output of system

# Alarm Example

- States:


- Power-Up: 00
- Init: 01
- Wait: 10
- Alarm: 11

- Inputs:

- A: Arm the alarm
- B: Sensor detection

- Output:

- Z: Alarm sound

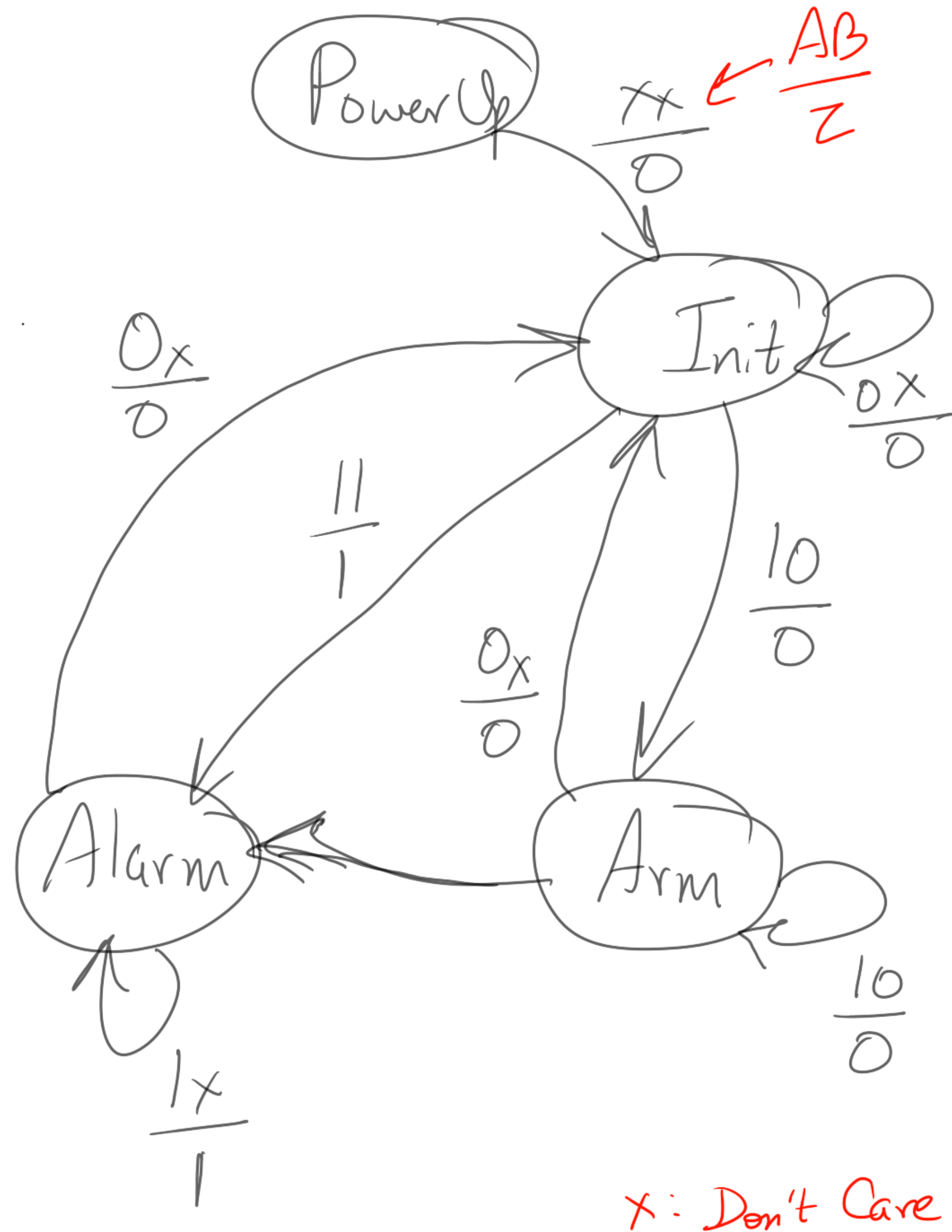

# Alarm Example




## Truth Table

$Q_{old}^{(1)}$	$Q_{old}^{(0)}$	A	B	$Q_{new}^{(1)}$	$Q_{new}^{(0)}$	Z
0	0	0	0	0	1	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	1
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	1	1	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

# Alarm Example
   
## K-Maps


- $Q_{new}(1) = Q_0A + Q_1A$
- $Q_{new}(0) = Q_1'Q_0' + A' + Q_1Q_0 + B$
- $Z = Q_0AB + Q_1Q_0A + Q_1AB$
- 



# Alarm Example
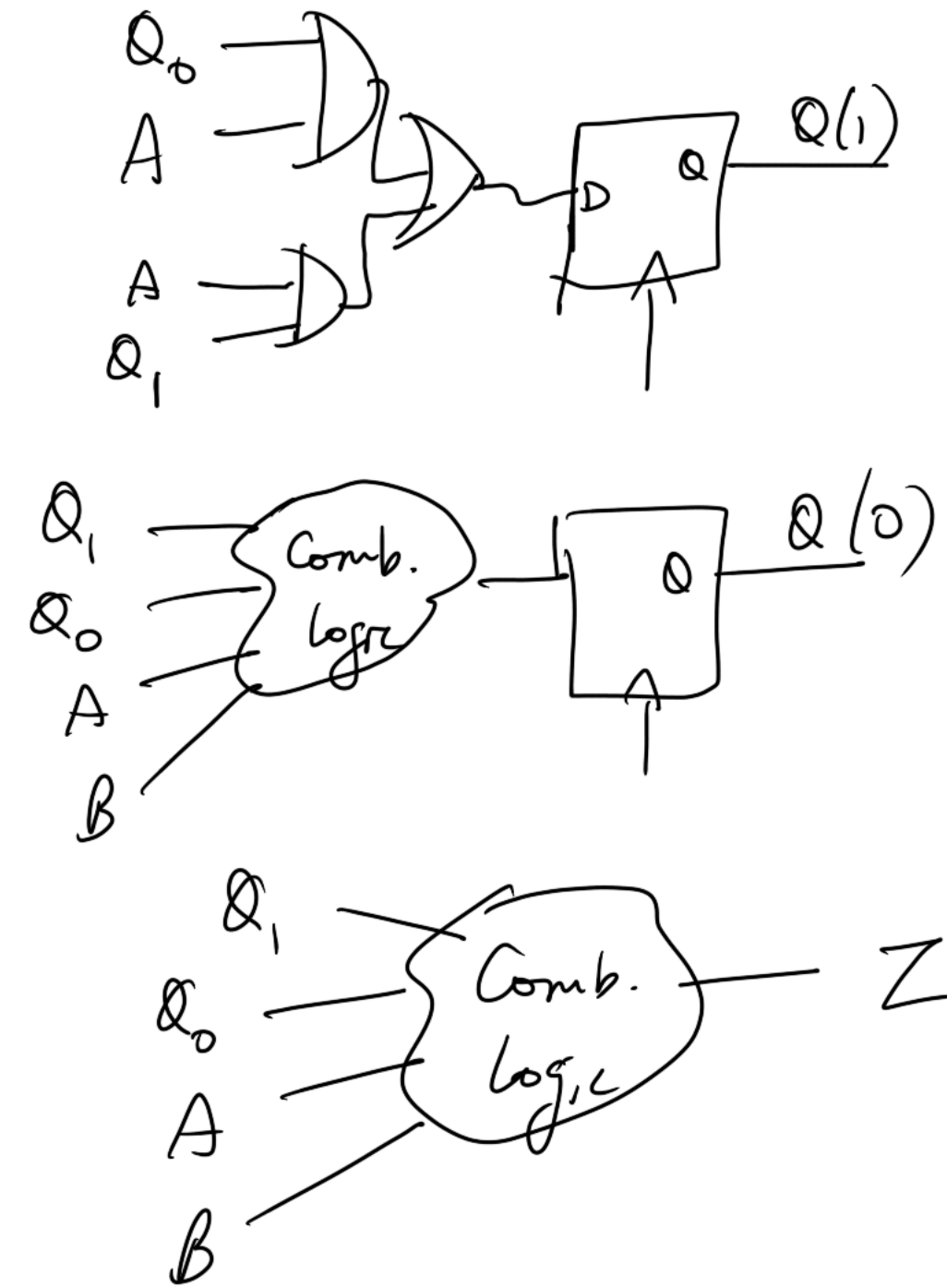
## Block Diagram

- $Q_{\text{new}}(1) = Q_0A + Q_1A$
- $Q_{\text{new}}(0) = Q_1'Q_0' + A' + Q_1Q_0 + B$
- $Z = Q_0AB + Q_1Q_0A + Q_1AB$
- 






# Alarm Example
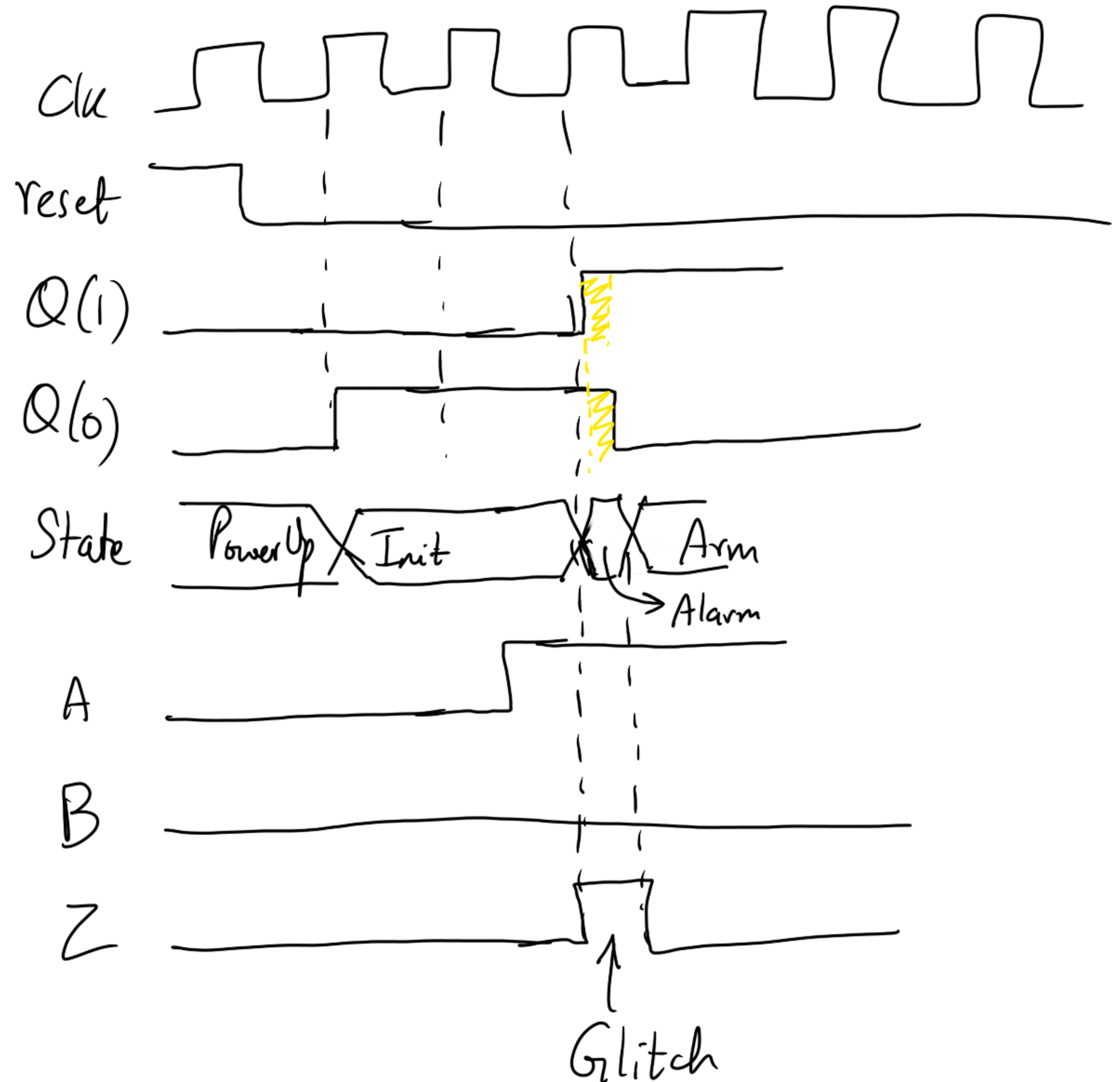
## Glitch

- Transition of A: 0->1 with state 01
  - Bit 0: 1->0
  - Bit 1: 0->1
- State: 01 -> 11 -> 10
  - State bits are independent
  - State could erroneously go to Alarm state for a brief period



# Alarm Example

## Ways to avoid glitch

- Register the output
  - Add a flip-flop for Z
- Gray code for state assignment
  - Problem caused because both bits of state changed when transitioning from Init -> Arm
  - Allow only bit of state to change for transitions to avoid problem
    - PowerUp: 000
    - Init: 001
    - Arm: 011
    - Alarm: 101
    - Add an extra state to transition from Arm to Alarm with value of 111

# Moore vs Mealy FSM

- Mealy: output depends on both state and input
- Moore: output only depends on state
  - Changes/Glitches in input doesn't affect output
  - Simpler design than Mealy
    - Changes in input take time to reflect on output

# Alarm Example

## Moore FSM

- States:

- Power-Up: 00
- Init: 01
- Wait: 10
- Alarm: 11

- Moore:

- $Z = Q_1Q_0$
- Only depends on state

- Mealy:

- $Z = Q_0AB + Q_1Q_0A + Q_1AB$
- Depended on both state and inputs

