

CMSC 313 HW4

Due 3/7/2024 11:59pm

Please submit the completed homework through Blackboard.

There are two 4-bit unsigned values A ($A_3A_2A_1A_0$) and B ($B_3B_2B_1B_0$) provided as input with a maximum value of 7. So A_3 and B_3 will be 0.

The objective of this homework is to determine the equations for two output bits ZF and SF. The ZF bit should be 1 if $A=B$. The SF bit should be 1 if $B>A$.

The homework can be broken down into the following steps:

1. Calculate the equations for determining the 1's complement of B . The inputs of this step are $B_3B_2B_1B_0$ and the outputs of this step are $O_3O_2O_1O_0$. Hint: O_0 only depends on B_0 , O_1 only depends on B_1 , etc. It is not necessary to do truth table.
2. Calculate the equations for determining $-B$. This is the 2's complement of B . The inputs of this step are $O_3O_2O_1O_0$ and the outputs of this step of $N_3N_2N_1N_0$. The 2's complement of a number is found by adding 1 to the 1's complement of the number. So we are adding $O_3O_2O_1O_0$ and 0001. Refer to the below table from the first lecture about adding 2 numbers. For the first bit, the input A in the table is O_0 and the input B in the table is 1. The sum is N_0 . N_0 is 1 if O_0 is 0. The carry-out C_1 is 1 if O_0 is 1. For the second bit, the input A in the table is O_1 and the input B in the table is C_1 . The sum is N_1 . N_1 is 1 if $O_1C_1' + O_1'C_1$. C_2 is 1 if O_1C_1 . Similarly, calculate the equations for N_2 , C_3 , N_3 . The equations can be left as function of the inputs of this step ($O_3O_2O_1O_0$); it is not necessary to calculate them as function of B ($B_3B_2B_1B_0$).

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

3. Calculate $A-B$. The inputs for this step are A ($A_3A_2A_1A_0$) and $-B$ ($N_3N_2N_1N_0$). The outputs for this step are S ($S_3S_2S_1S_0$). For the first bit, the input A is A_0 and the input B is B_0 . The sum S_0 is 1 if $A_0B_0' + A_0'B_0$ from the table above. The carry-out C_1 is 1 if A_0B_0 . For the second bit, however, there are 3 inputs: A_1 , B_1 , C_1 . We have to use the full adder to calculate the sum and carry-out. Refer to the table that we studied in the first lecture below. In our case, the input A is A_1 , input B is B_1 and carry-in input is C_1 . The sum S_1 is 1 if $A_1 \oplus B_1 \oplus C_1$ (i.e., A_1 xor B_1 xor C_1 : odd number of inputs are 1). The carry-out C_2 is 1 if $A_1B_1 + A_1C_1 + B_1C_1$. Similarly calculate S_2 , C_3 , S_3 . The equations can be left as function of the inputs of this step: A and N .

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

4. Calculate ZF output from S ($S_3S_2S_1S_0$). Write the equation for ZF in terms of the input S.
5. Calculate SF output from S ($S_3S_2S_1S_0$). Write the equation for SF in terms of the input S.