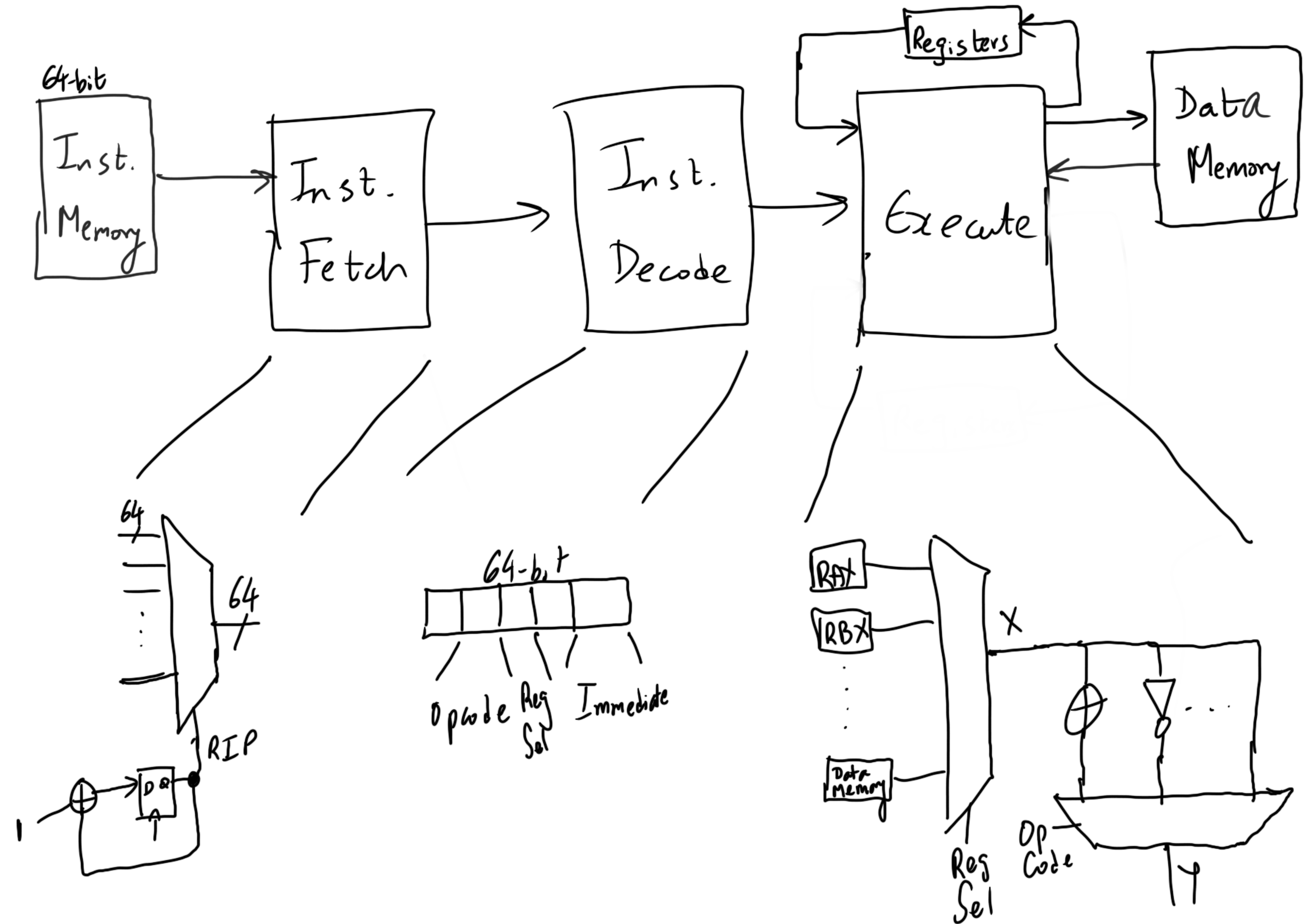



# Processor Pipelining

# Processor Overview


 
# Register input requirements



- D register
  - D input latched just before clk rising edge





# Positive-Edge Master-Slave D Flip-Flop
  
## Setup Time

- D input need to be stable before C rising edge
- Race condition between D and C
- Avoid uncertainty of output





# Signals example

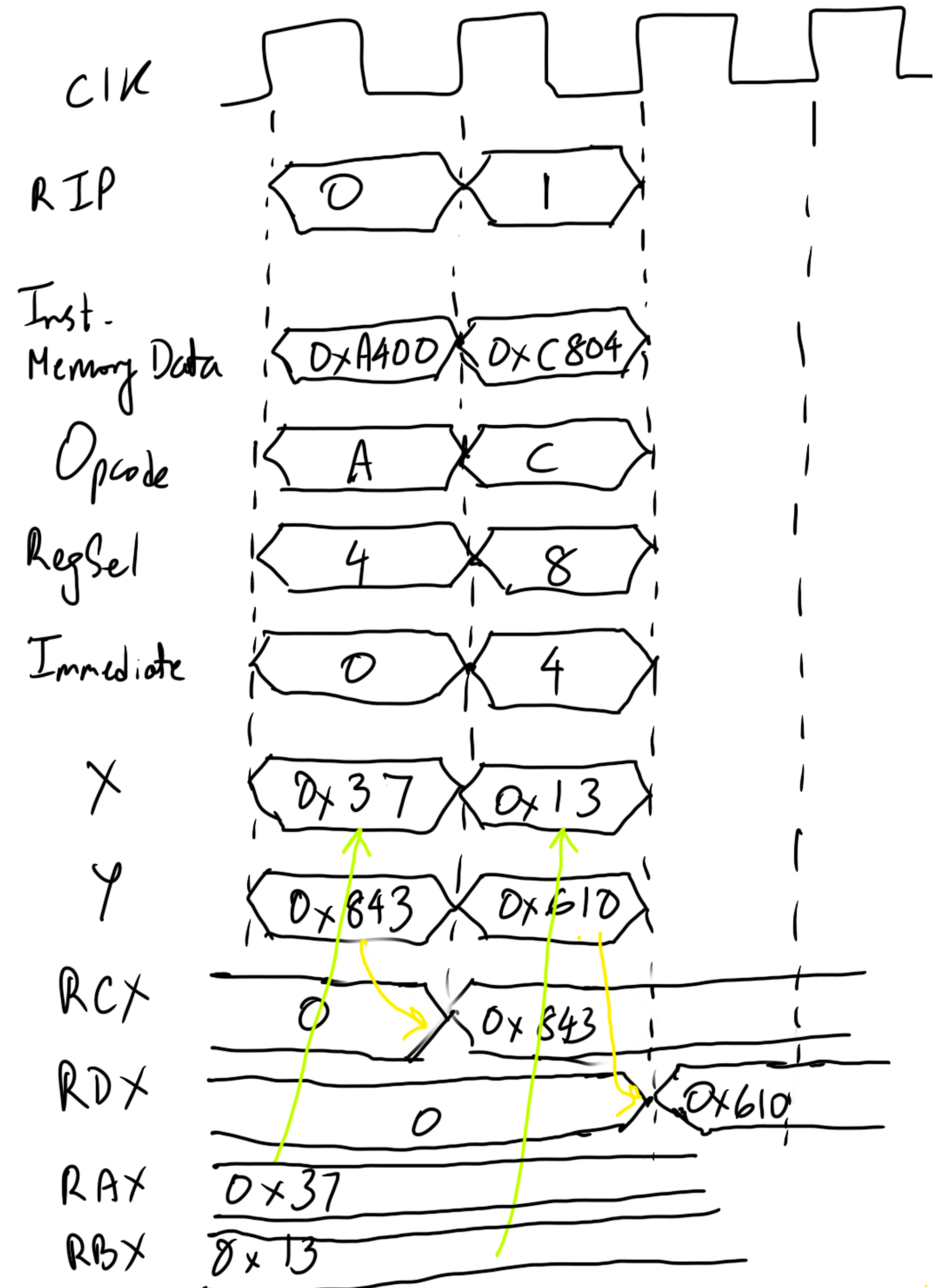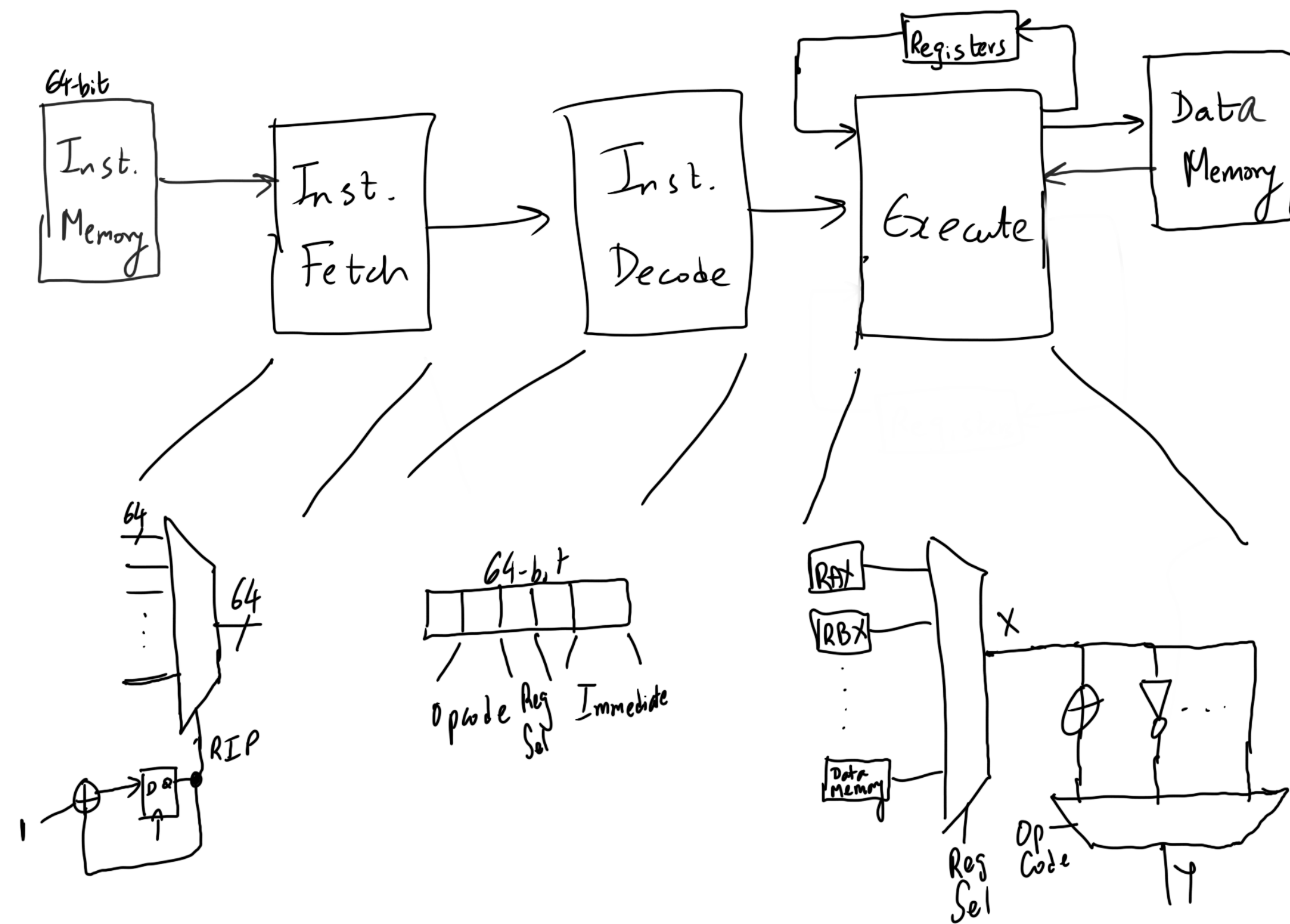


# Positive-Edge Master-Slave D Flip-Flop

## Timing Diagram with Propagation Delay

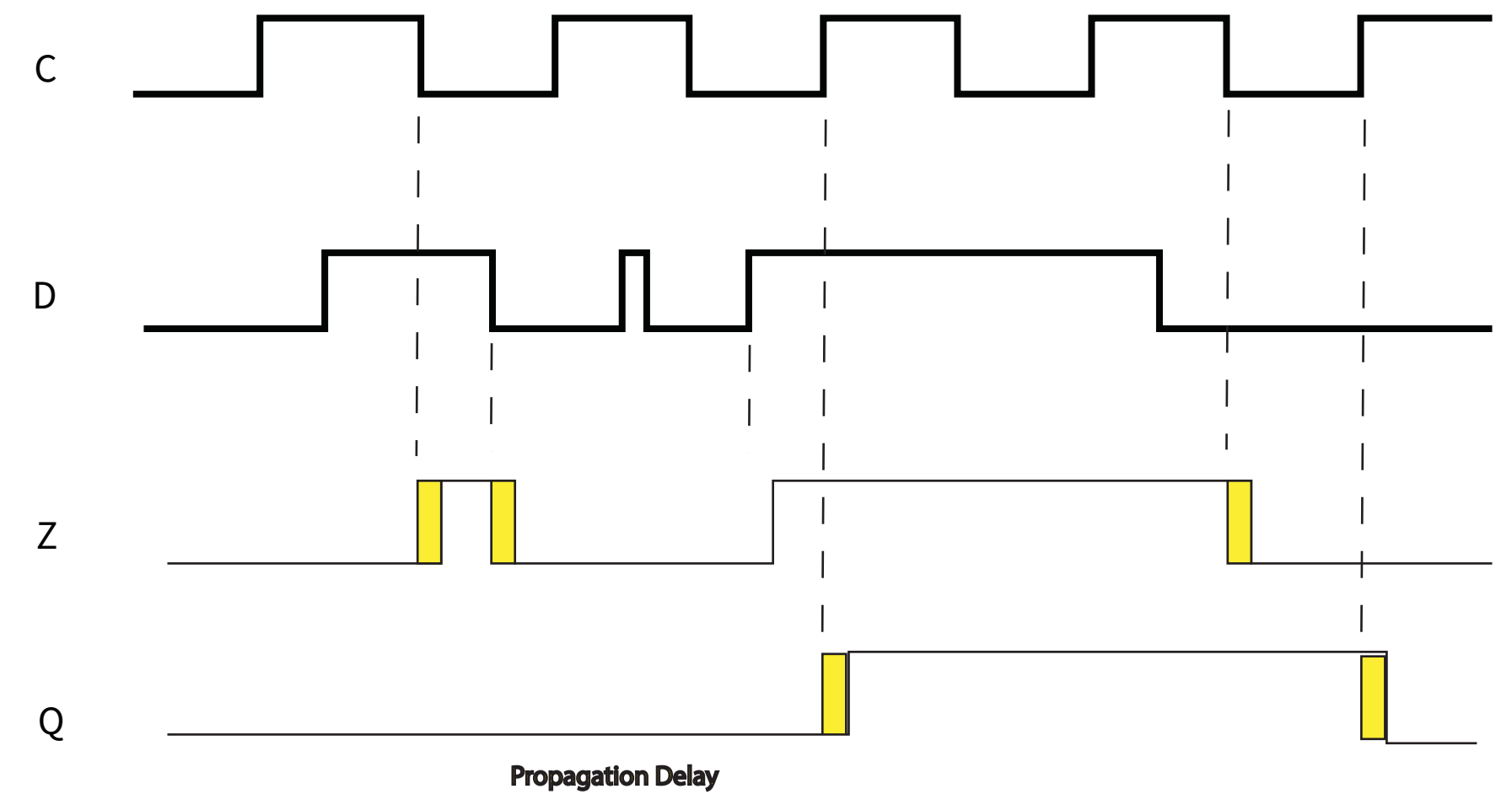 
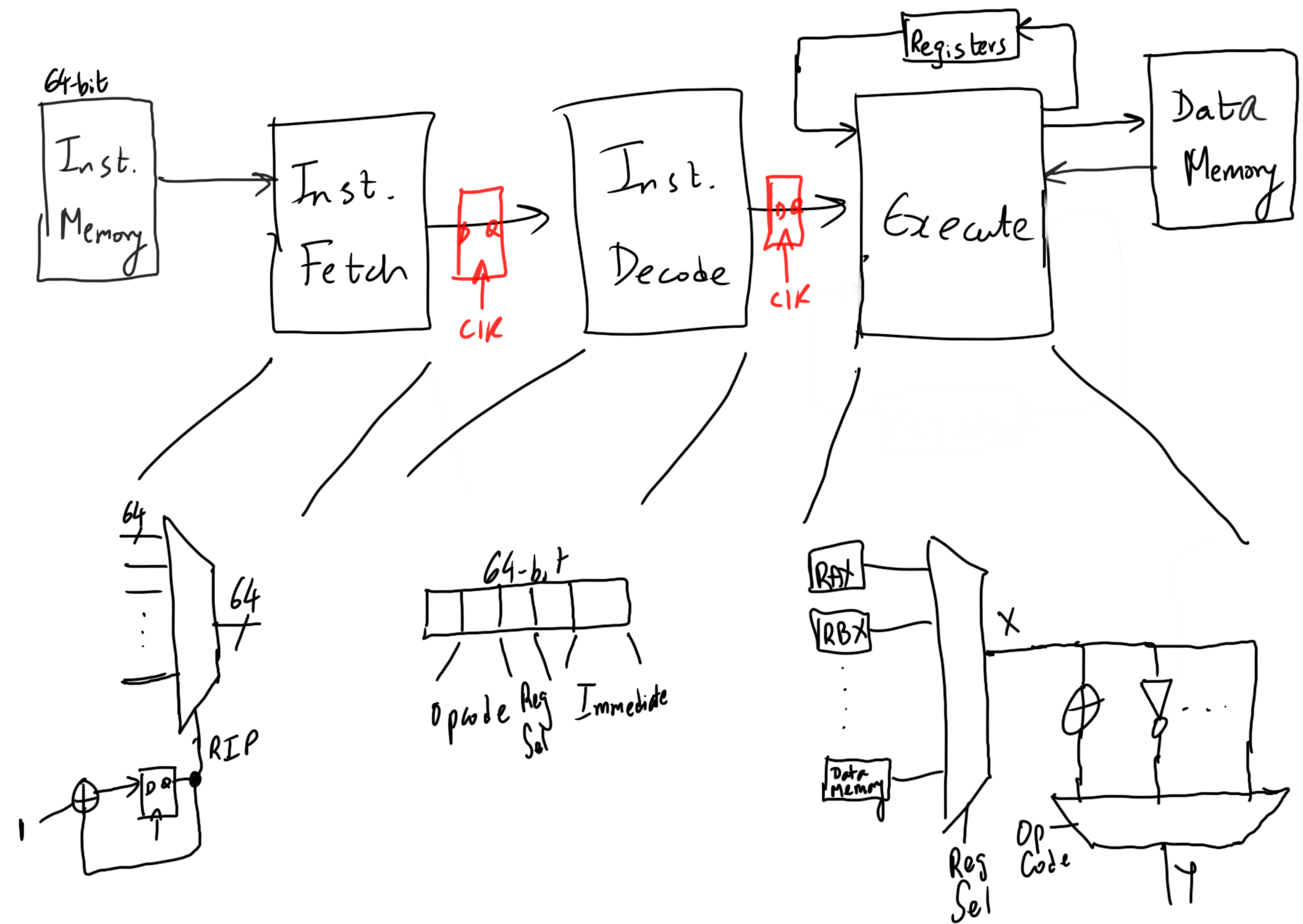
# Pipelining

- Need to add registers in data path to reduce propagation delay in each clock cycle





# Clock Frequency of Processor

- Trade-off between more complex operation performed in a clock cycle vs. faster clock frequency
- Example of a complex operation vs simple operation
  - Stages all combined together
  - Addition of 64 bits vs. Addition of 16 bits



# Hazards/Dependency

- Read After Write
- Conditional Jump
- Especially true with more pipeline stages (x86 64 versions have more than 12)
  - Needed to run the clock at faster frequency