

CMSC 313 Quiz 1

Name (please print clearly):

2 problems (front and back of this sheet).

No electronics allowed.

1.

We are given a value in signed magnitude form as input. The inputs are the magnitude of the value and the sign bit of the value.

Let A be the 2-bit magnitude:

- $A_1A_0 = 00$ in binary: represents magnitude of 0 in decimal
- $A_1A_0 = 01$ in binary: represents magnitude of 1 in decimal
- $A_1A_0 = 10$ in binary: represents magnitude of 2 in decimal
- $A_1A_0 = 11$ in binary: represents magnitude of 3 in decimal

Let S be the sign bit.

For example, if $A=2$ and $S=1$, the value is -2 . If $A=1$ and $S=0$, the value is $+1$.


Compute the equations for converting the signed magnitude value to 2's complement value (supporting range from -3 to $+3$). In 2's complement form, there needs to be 3 bits for the output value. Let $Z = Z_2Z_1Z_0$ be the 3-bit 2's complement value output. Just the equations for each of the 3 output bits are sufficient; no need to draw the circuit diagram or a timing diagram. In other words, write Z_2 as $f(A_1, A_0, S)$, Z_1 as $g(A_1, A_0, S)$, Z_0 as $h(A_1, A_0, S)$.

Hint: For an input value of -2 , $Z=110$ (2 in decimal is 010 in binary. 1's complement of 2 is 101. Adding 1 to it gives 110). For an input value of $+1$, $Z=001$ (no need to perform 2's complement for a positive number).

2nd Hint: In signed magnitude form, 0 can be represented as $+0$ ($A=0$ and $S=0$) or as -0 ($A=0$ and $S=1$).

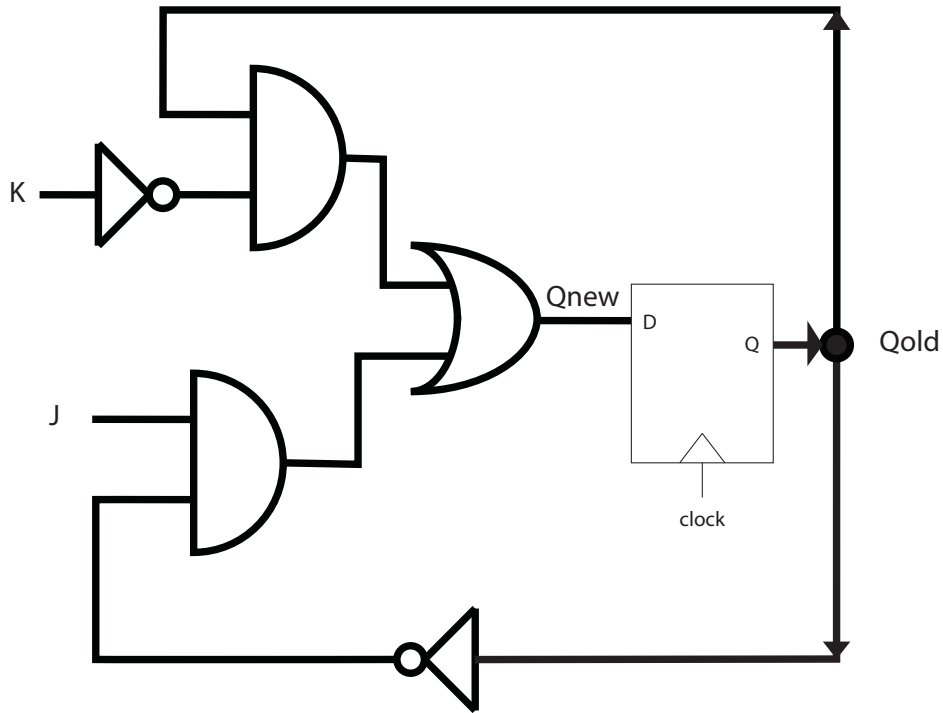2.

For the circuit given below, write the truth table. Give a brief explanation of how J and K inputs affect the output (i.e., how is Q_{new} related to Q_{old} when $JK=00, 01, 10$ and 11 ?).



Hint: The inputs are Q_{old}, J, K (8 rows in truth table). The output is Q_{new} .