

Sequential Logic

Overview

Part 1

- K-Maps with Don't Care midterms
- Combinational and Sequential Logic
- Inputs, Outputs and States
- Set Latch
- Reset Latch
- SR Latch
 - Feedback with NOR gates
 - Timing Diagram
 - Truth Table and K-Map
 - Feedback with NAND gates
- Gated SR and Gated Delay Latches
 - Wrapper on SR Latch
 - Truth Table and K-Map
 - Feedback Logic

Overview

Part 2

- Master-Slave SR Flip Flop
 - Circuit
 - Timing Diagram
- Master-Slave D Flip Flop
 - Circuit
 - Timing Diagram
- Edge-Triggered Flip Flop
 - Propagation Delay
 - Setup/Hold Time

Overview

Part 3


- Counter
- Moore/Mealy State Machine Design
- Register File
- Memory

K-Maps

Don't Care minterms


- Some minterm outputs could be 0 or 1
 - Customer doesn't care
- Example:
 - A: 1 if temperature is greater than 80 degrees
 - B: 1 if temperature is greater than 70 degrees
 - C: 1 if sunny
 - Z=1 when Air Conditioning should be on
 - If $T > 80$, Turn on
 - If not sunny and $70 < T < 80$, Don't care
 - If sunny and temp. < 70 degrees, Don't care

A	B	C	Q
0	0	0	0
0	0	1	X (Don't Care)
0	1	0	X (Don't Care)
0	1	1	0
1	0	0	X (Invalid)
1	0	1	X (Invalid)
1	1	0	1
1	1	1	1

 

Combinational and Sequential Logic

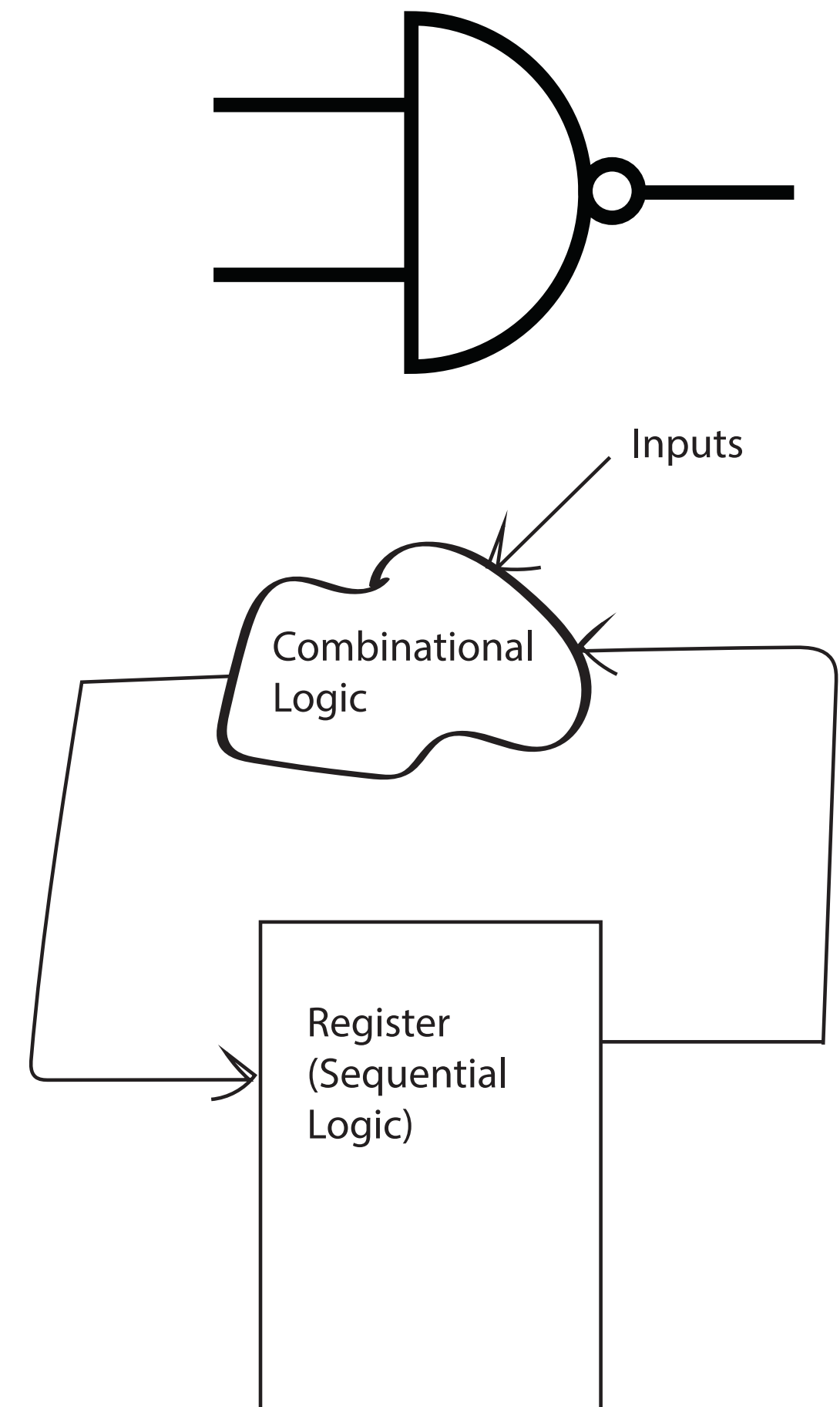- Combinational Logic
 - Logic gates (AND, OR, NOT, NAND, etc.)
 - Output depends only on input(s)
- Sequential Logic
 - Output depends on input(s) and/or current state of system
 - Store state
 - Retain value as long as power is present
 - Will look at memory in next lecture




Inputs, Outputs and States

- Inputs:
 - Thermometer reading (outside car): degrees Fahrenheit rounded to integer
 - Weather: Sunny (0), Cloudy (1), Windy (2), Rainy (3), Snowy (4), etc.
 - Desired inside temperature: degrees Fahrenheit rounded to integer
 - Thermometer reading (inside car): degrees Fahrenheit rounded to integer
 - Mode: Auto (0), A/C off (1), A/C on (2)
- State:
 - Current A/C level: 0-3
- Output:
 - Change A/C level: No change (0), Increase (1), Decrease (2)
 - Internal: changes value of “Current A/C level” state
 - LED screen: show current A/C level


Set Latch

 - S input == 1: force output to 1
 - OR gate input
- S input == 0: preserve output value
 - OR gate's 2nd input



Reset Latch

 
- R input == 1: force output to 0
 - R': AND gate's input
- R input == 0: preserve output value
 - Q: AND gate's 2nd input



SR Latch

Requirements and Timing Diagram

 - S input == 1: force output to 1
- R input == 1: force output to 0
- S and R inputs == 0: preserve output
- S and R inputs == 1:
 - Output cannot be both 1 and 0
 - Invalid entry
 - Don't care: Design can pick S or R





SR Latch

Truth Table & K-Map

- $Q_{\text{new}} = S + R'Q_{\text{old}}$



S	R	Q (Old)	Q (New)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

 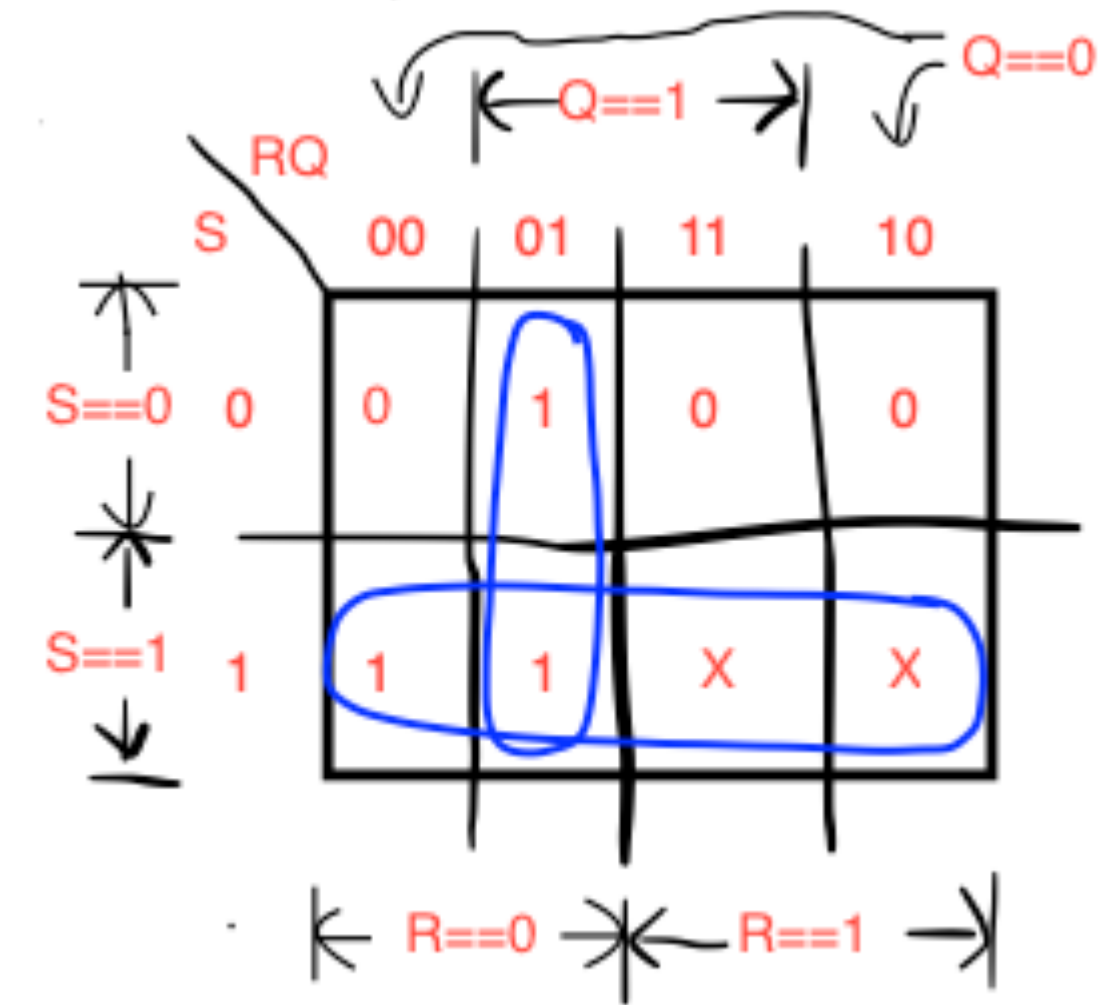

SR Latch

Design

 
 
- S input == 1: force output to 1
- R input == 1: force output to 0
- S and R inputs == 0: preserve output
- Use combination of S latch and R latch
- Re-arrange to use NOR gates
 - $AB = (A' + B')'$



SR Latch

Design



 
 
- S input == 1: force output to 1
- R input == 1: force output to 0
- S and R inputs == 0: preserve output
- Use combination of S latch and R latch
- Re-arrange to use NOR gates
 - $AB = (A' + B')'$
 - $A + B = (A'B')'$



SR Latch

NAND Gates

    
- $Q_{\text{new}} = S + R'Q_{\text{old}}$
- $A + B = (A'B')'$






Gated SR Latch

Requirements and Timing Diagram

 - **C input == 0: Don't allow any change to Q**
- **C input == 1: Allow Set/Reset**
- S input == 1: force output to 1
- R input == 1: force output to 0
- S and R inputs == 0: preserve output
- S and R inputs == 1:
 - Output cannot be both 1 and 0
 - Invalid entry
 - Don't care: Design can pick S or R




Gated SR Latch

   




Gated D Latch

Requirements and Timing Diagram

 - **C input == 0: Don't allow any change to Q**
- **C input == 1: Allow D input**
- D == 1 (S input == 1): force output to 1
- D == 0 (R input == 1): force output to 0
- ~~S and R inputs == 0: preserve output~~
 - Output preserved if C == 0
- ~~S and R inputs == 1:~~
 - Invalid entry



Gated D Latch

   

Latch Feedback Issue

- Input:
 - $A=0$: No change
 - $A=1$: Invert state
- $A=1$ and $C=1$:
 - Instantaneous oscillation of Q without gap/stop

